

8	(a) P shown between earth symbol and voltmeter	B1	[1]
	(b) (i) $\text{gain} = (50 \times 10^3) / 100 = 500$	C1	
	$V_{\text{IN}} (= 5.0 / 500) = 0.010 \text{ V}$	A1	[2]
	(ii) $V_{\text{IN}} (= 5.0 / 5.0) = 1.0 \text{ V}$	A1	[1]
	(c) e.g. multi-range (volt)meter c.r.o. sensitivity control amplifier channel selector	B1	[1]