

6(a)	Any valid two points e.g.: • to store (electrical) energy • smoothing/reduce ripple (on direct voltages/currents) • to block d.c. • timing/time delay (circuits) • in oscillator (circuits) • in tuning (circuits) • to prevent arcing/sparks	B2
6(b)	clear indication of equal charge on each capacitor	B1
	$E = V_1 + V_2 + V_3$ and $V = Q/C$	M1
	completion of algebra leading to $1/C = 1/C_1 + 1/C_2 + 1/C_3$	A1
6(c)(i)	three capacitors connected in parallel	B1
6(c)(ii)	parallel combination of three capacitors connected in series with one capacitor	B1

Question	Answer	Marks
----------	--------	-------