

9(a)(i)	relay coil shown connected between diode and earth	B1
	switch shown connected across lamp	B1
9(a)(ii)	Any one from: • (for diode to conduct) current flow is into output of op-amp • when earth is at higher potential diode is forward biased • diode blocks current when output positive • diode must conduct	M1
	so V_{OUT} is negative	A1
9(b)(i)	strain gauge	B1
9(b)(ii)	light-dependent resistor	B1