

Question	Answer	Marks
7(a)	the constant / direct current (in a resistor)	M1
	that causes the same <u>mean</u> power dissipation as the alternating current	A1
7(b)(i)	mean power = 3.2 W	A1
7(b)(ii)	$P = I^2 R$	C1
	$I_{\text{RMS}} = \sqrt{(3.2 / 26)} \text{ or } [\sqrt{(6.4 / 26)}] / \sqrt{2}$ = 0.35 A	A1
7(c)(i)	diode	B1
7(c)(ii)	<u>sketch:</u> <i>either:</i> line showing $P = 0$ between $t = 0$ and $t = 0.0125 \text{ s}$ and between $t = 0.0375 \text{ s}$ and $t = 0.050 \text{ s}$ and non-zero P in between	M1
	<i>or:</i> line showing $P = 0$ between $t = 0.0125 \text{ s}$ and $t = 0.0375 \text{ s}$, and non-zero P either side	
	line in non-zero P regions with correct sine ² shape, sitting on the t -axis, with maximum P at 6.4 W	A1
7(c)(iii)	mean power is now half of what it was before rectification	B1
	$I_{\text{RMS}} = \sqrt{(1.6 / 26)}$ = 0.25 A	A1