

6 (a) State what is meant by an electric current.

.....
..... [1]

(b) A cell has electromotive force (e.m.f.) 1.50 V and internal resistance $0.75\ \Omega$.

On Figure 6.1, draw the variation of the terminal potential difference (p.d.) with current in the cell for current between 0 A and 1.6 A.

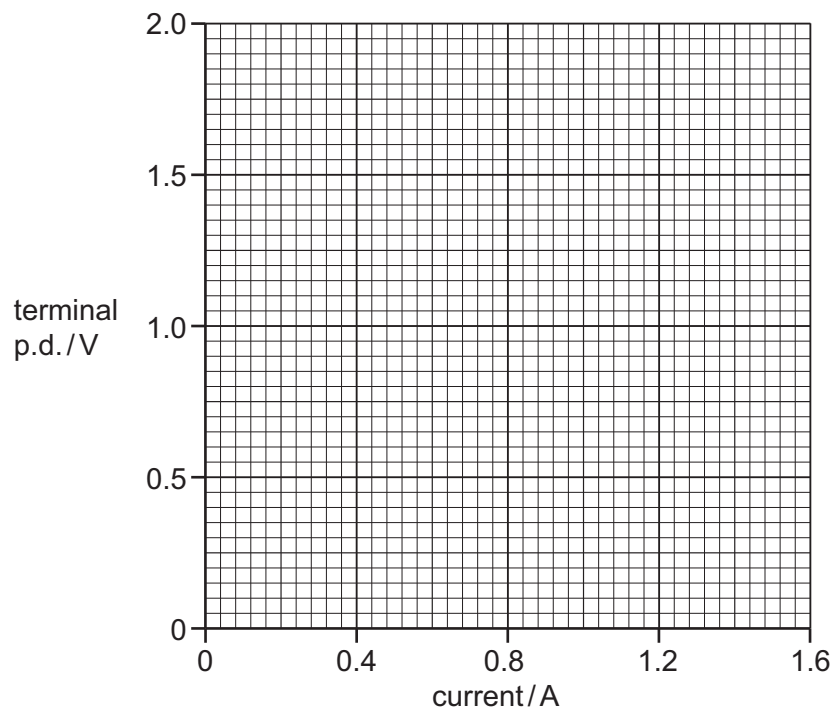


Figure 6.1

[2]

- (c) A metal wire X has length 6.8 m and cross-sectional area $2.0 \times 10^{-7} \text{ m}^2$. The resistance of the wire is 0.82Ω .

The wire is connected to a circuit containing the cell in 6(b) and a fixed resistor of resistance R , as shown in Figure 6.2.

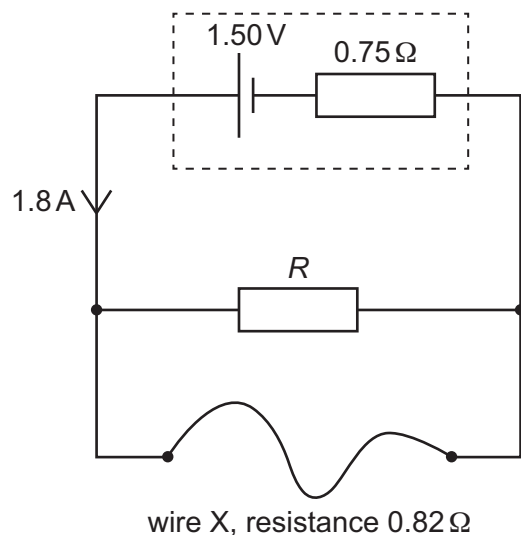


Figure 6.2

The current in the cell is 1.8 A.

- (i) Calculate the resistivity ρ of the metal from which wire X is made.

$$\rho = \dots\dots\dots \Omega \text{ m} \quad [2]$$

- (ii) Calculate R .

$$R = \dots\dots\dots \Omega \quad [3]$$

* 0000800000015 *

DFD



15



(iii) Calculate the power dissipated in the internal resistance of the cell.

power = W [2]

[Total: 10]