

Question	Answer	Marks
6(a)(i)	lamp needs 'high' power/'large' current/'large' voltage	B1
	op-amp can deliver only a small current/small voltage	B1
6(a)(ii)	correct symbol for relay coil connected between output and earth	B1
	switch between mains supply and lamp	B1
6(b)(i)	vary light intensity at which lamp is switched on/off	B1
6(b)(ii)	so that relay operates for only one current/voltage direction or so that relay/lamp operates for either dark or light conditions	B1
6(c)	when light level increases, LDR resistance decreases	B1
	(R_{LDR} low,) so $V^- > V^+$, so V_{OUT} negative/ -5 V (must be consistent with B1 mark)	M1
	or	
	when light level decreases, LDR resistance increases	(B1)
	(R_{LDR} high,) so $V^- < V^+$, so V_{OUT} is positive/ $+5\text{ V}$ (must be consistent with B1 mark)	(M1)
	lamp comes on as light level decreases or lamp goes off as light level increases	A1