

- 32** Which graph represents the variation with current I of potential difference (p.d.) V for a filament lamp?

