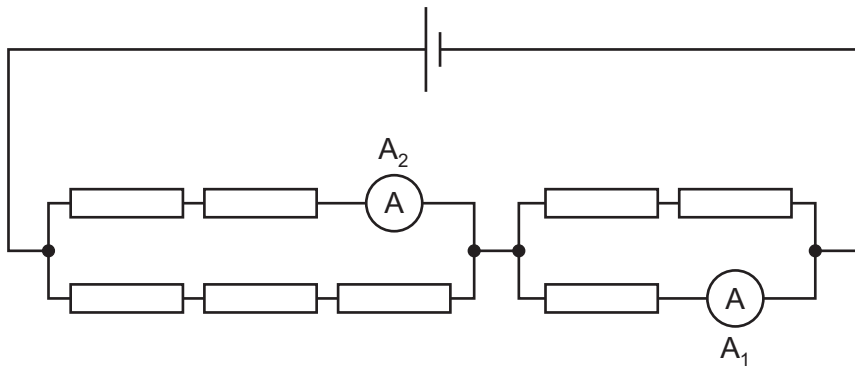


36 Eight identical resistors are connected as shown.



Ammeter A_1 reads 1.50 A.

What is the reading on ammeter A_2 ?

A 0.75 A

B 0.90 A

C 1.35 A

D 1.50 A