

Question	Answer	Marks	Guidance
5(a)	$I_T = I_1 + I_2 + I_3$ either $(V/R_T) = (V/R_1) + (V/R_2) + (V/R_3)$ or $(I_T/V) = (I_1/V) + (I_2/V) + (I_3/V)$	B1	Throughout allow I and R without subscript to mean I_T and R_T respectively, and allow V_T for V
	<u>and</u> $1/R_T = 1/R_1 + 1/R_2 + 1/R_3$	B1	If uses V_1, V_2, V_3 must also explicitly state that $(V =) V_1 = V_2 = V_3$. For the second mark, the associated working <u>and</u> final answer must both be shown A fully correct answer in terms of two rather than three resistors credit 1/2
5(b)(i)	$R_{(T)} = (1/2.8 + 1/2.8)^{-1}$ $= 1.4$ current in battery = $V/R_{(T)}$ $= 12/1.4$	C1	Allow any correct expression for the parallel combination e.g. $1/R_{(T)} = 1/2.8 + 1/2.8$ or $R_{(T)} = (2.8 \times 2.8)/(2.8 + 2.8)$
	$= 8.6 \text{ A}$	A1	
	OR $I = 12/2.8$ $= 4.3$	(C1)	
	current in battery = $4.3 + 4.3$ $= 8.6 \text{ A}$	(A1)	<u>Special case:</u> A final answer of 4.3 A without any supporting working credit 1/2

Question	Answer	Marks	Guidance
5(b)(ii)	$v = I / Anq$ $= (8.6 / 2) / (6.1 \times 10^{-6} \times 8.5 \times 10^{28} \times 1.6 \times 10^{-19})$	C1	no mark for symbol formula as given in the formula sheet ECF current from 5(b)(i) Allow $(12 / 1.4) / (2 \times 6.1 \times 10^{-6} \times 8.5 \times 10^{28} \times 1.6 \times 10^{-19})$ if treats as a single wire of double area
	$= 5.2 \times 10^{-5} \text{ m s}^{-1}$	A1	<u>Special case:</u> candidates that do not half their current from 5(b)(i) can be credited 1 / 2 if working is shown e.g. $= 8.6 / (6.1 \times 10^{-6} \times 8.5 \times 10^{28} \times 1.6 \times 10^{-19})$ $= 1.0 \times 10^{-4} \text{ m s}^{-1}$
5(c)(i)	light-dependent resistor	B1	Allow LDR
5(c)(ii)	$I_{(X)} = 5 - 12 / 2.8$ $= 0.71$	C1	Allow $I_{(X)} = 5 - (8.6 / 2)$ ($= 0.70$) and allow ECF of current from 5(b)(i)
	$R_{(\text{top branch})} = 12 / 0.71$ $= 16.8$	C1	
	$R_{(X)} = 16.8 - 2.8$ $= 14 \Omega$	A1	
	OR $I_{(X)} = 5 - 12 / 2.8$ $= 0.71$	(C1)	Allow $I_{(X)} = 5 - (8.6 / 2)$ ($= 0.70$) and allow ECF of current from 5(b)(i)
	$V_{(\text{resistance wire})} = 0.71 \times 2.8$ $= 2.0$ $V_{(X)} = 12 - 2.0$ $= 10$	(C1)	
	$R_{(X)} = 10 / 0.71$ $= 14 \Omega$	(A1)	

Question	Answer	Marks	Guidance
5(c)(ii)	OR $R_{(T)} = 12 / 5$ $= 2.4$	(C1)	
	$1 / 2.4 = 1 / 2.8 + 1 / R_{(\text{top branch})}$ $R_{(\text{top branch})} = 16.8$	(C1)	Allow $1 / 2.4 = 1 / 2.8 + 1 / (2.8 + R_{(X)})$
	$R_{(X)} = 16.8 - 2.8$ $= 14 \Omega$	(A1)	
5(c)(iii)	(current in battery decreased, total resistance increased,) resistance (of X) increased	M1	Allow 'LDR' instead of X Allow V, I, R to mean potential difference, current and resistance respectively Allow ↓ for decreases and ↑ for increases (BOD) Ignore all comments about p.d. and emf
	light intensity (incident on X) decreased	A1	Allow '(environment is) darker / dimmer / less light / less bright' Allow 'temperature (of X/LDR) has decreased'