

8	(a) decreases gain increases bandwidth / decreases distortion / increases (operating) stability	B1 B1	[2]
(b)	(i) additional resistor connected between $7.2\text{ k}\Omega$ resistor and earth V^- joined to lower end of $7.2\text{ k}\Omega$ resistor <u>and</u> V^+ joined to V_{IN}	B1 B1	[2]
	(ii) either $5 = 1 + (7.2/R)$ or $5 = 1 + (7200/R)$ $R = 1.8\text{ k}\Omega$	C1 A1	[2]
	(iii) horizontal line from (0, 8.0) to (1.8, 8.0) straight line from (1.8, 8.0) to (5.0, 0)	B1 B1	[2]

(allow a tolerance of $\pm \frac{1}{2}$ small square when marking the graph)

Page 5	Mark Scheme	Syllabus	Paper
	Cambridge International AS/A Level – March 2016	9702	42