

7 (a) charge exists only in discrete amounts B1 [1]

(b) (i) $E = I(R + r)$ or $V = IR$ C1

(total resistance =) $2.7 + 0.30 + 0.25 (= 3.25 \Omega)$ M1

$I = 9.0 / (2.7 + 0.30 + 0.25)$ or $9.0 / 3.25 = 2.8 \text{ A}$ A1 [3]

(ii) $V = IR_{\text{ext}}$ C1
 $= 2.77 \times 3.0$ or 2.8×3.0

or

$V = E - Ir$ (C1)
 $= 9.0 - 2.77 \times 0.25$ or $9.0 - 2.8 \times 0.25$

$V = 8.3 (8.31) \text{ V}$ or 8.4 V A1 [2]

(c) (i) $I = nevA$

$v = 2.77 / (8.5 \times 10^{29} \times 1.6 \times 10^{-19} \times 2.5 \times 10^{-6})$ M1

$= 8.1 (8.147) \times 10^{-6} \text{ ms}^{-1}$ or $8.2 \times 10^{-6} \text{ ms}^{-1}$ A1 [2]

(ii) A reduces by a factor 4 (1/4 less) or resistance of Z goes up by 4× M1

current goes down but by less than a factor of 4 (as total resistance does not go up by a factor of 4) so drift speed goes up A1 [2]