

11 (a)	point P shown at 'lower end' of load	B1	[1]
(b)	$V_{\text{r.m.s.}} = 6.0/\sqrt{2} = 4.24 \text{ V}$	C1	
	$I_{\text{r.m.s.}} = 4.24/(2.4 \times 10^3)$ $= 1.8 \times 10^{-3} \text{ A}$	A1	[2]
(c) (i)	capacitor in parallel with load	B1	[1]
(ii)	line from peak to curve at 3.0 V for either half- or full-wave rectified	M1	
	correct curvature on line (gradient becoming more shallow)	A1	
	line drawn as for full-wave rectified	A1	[3]

Page 7	Mark Scheme	Syllabus	Paper
	Cambridge International AS/A Level – May/June 2016	9702	42