

8	(a) (i) gain = <u>voltage</u> output/ <u>voltage</u> input	B1	[1]
	(ii) changes in V_{OUT} occur immediately when V_{IN} changes	M1 A1	
	or		
	changes in V_{IN} result in immediate changes to V_{OUT}	(M1) (A1)	[2]
	(b) $12 = 1 + R/(1.5 \times 10^3)$	C1	
	$R = 16.5 \text{ k}\Omega$	A1	[2]
	(c) straight line from (0,0) to (0.75 t_1 , 9.0 V)	B1	
	horizontal line from endpoint of straight line to t_1	B1	
	+9 V to -9 V (or v.v.) at t_1	B1	
	correct line to t_2	B1	[4]

Page 6	Mark Scheme	Syllabus	Paper
	Cambridge International AS/A Level – May/June 2016	9702	42