

Question	Answer	Marks
7(a)	equal and opposite charges on the plates so no resultant charge	B1
	+ve and –ve charges separated so energy stored	B1
7(b)	charge / potential difference	M1
	reference to charge on one plate and p.d. between plates	A1
7(c)	energy = $\frac{1}{2} CV^2$ or energy = $\frac{1}{2} QV$ and $C = Q / V$	C1
	$(1 / 16) \times \frac{1}{2} CV_0^2 = \frac{1}{2} CV^2$ $V = \frac{1}{4} V_0$	A1

9702/42

Cambridge International AS/A Level – Mark Scheme

May/June 2017

PUBLISHED

Question	Answer	Marks
8(c)(i)	circle around both diodes	B1