

Question	Answer	Marks
7(a)	<u>sum of</u> current(s) in(to) junction = <u>sum of</u> current(s) out of junction or (algebraic) sum of current(s) at a junction is zero	B1
7(b)(i)	1. potential difference = 0	A1
	2. potential difference = 9.6 V	A1
7(b)(ii)	for resistance in parallel: $(1/R_T) = (1/400) + (1/400)$ $R_T = 200(\Omega)$	C1
	$V/9.6 = 200/600$	C1
	$V = 3.2\text{ V}$	A1