

Question	Answer	Marks
7(a)	$R = \rho L / A$	C1
	$= (1.12 \times 10^{-6} \times 1.5) / 2.45 \times 10^{-7}$	C1
	$= 6.86 \, \Omega$	A1
7(b)(i)	(A method where the) reading (on the galvanometer) is zero.	B1

Question	Answer	Marks
7(b)(ii)	$\text{e.m.f.} / 1.2 = 64 / 150$	C1
	$\text{e.m.f.} = (64 / 150) \times 1.2$ $= 0.51 \text{ V}$	A1
7(b)(iii)	(the internal resistance will cause a) drop in p.d. across the wire / the terminal p.d. is lower	B1
	So the null point will move to the right	B1

Question	Answer	Marks