

Question	Answer	Marks
5(a)(i)	potential difference per unit current	B1
5(a)(ii)	resistor connected to cell in a closed loop and correct circuit symbols used for all components	B1
	ammeter connected in series with resistor and voltmeter connected in parallel with resistor	B1
5(b)(i)	(resistance) = $1.38 / 0.276 = 5.00 \text{ } (\Omega)$	A1
5(b)(ii)	$\rho = RA / L$	C1
	$\rho = 5.00 \times \pi \times (0.496 \times 10^{-3})^2 / (4 \times 0.864)$	C1
	$= 1.12 \times 10^{-6} \text{ } \Omega \text{ m}$	A1
5(b)(iii)	calculation of a fractional or percentage uncertainty in one quantity $0.001 / 0.864$ or $0.002 / 0.496$ or $0.02 / 1.38$ or $0.001 / 0.276$	C1
	percentage uncertainty = $[(0.001 / 0.864) + (2 \times 0.002 / 0.496) + (0.02 / 1.38) + (0.001 / 0.276)] \times 100$ $= 2.7\%$	A1
5(b)(iv)	$\Delta\rho = 0.03 \times 1.12 \times 10^{-6}$ $= 3 \times 10^{-8} \text{ } \Omega \text{ m}$	A1

9702/24

Cambridge International AS & A Level – Mark Scheme

October/November 2025

PUBLISHED

Question	Answer	Marks