

Question	Answer	Marks	Guidance
7(a)(i)	allows the current (unhindered) in one direction	B1	Allow 'converts a.c. into d.c.'
	blocks the current (completely) in the other direction	B1	
7(a)(ii)	diode shown connecting the wires in one gap, and direct connection across the other gap	B1	Allow two diodes if in consistent directions Allow a single diode in parallel with resistor Ignore a capacitor in parallel with resistor Do not allow if there any other components added into the circuit that would stop the circuit from working as a rectification circuit.
	correct symbol used for diode	B1	Ignore presence / absence of circle and / or line through the triangle. If more than one diode in circuit, all must have the correct symbol
7(b)	V_1 unrectified: r.m.s. voltage shown as $V_0 / \sqrt{2}$	B1	
	V_2 unrectified: r.m.s. voltage shown as V_0	B1	
	V_1 rectified: r.m.s. voltage shown as $V_0 / 2$	B1	
	V_2 rectified: r.m.s. voltage shown as $V_0 / \sqrt{2}$	B1	