

6	(a) either $P \propto V^2$ or $P = V^2/R$ C1 reduction = $(230^2 - 220^2)/230^2$ = 8.5 % A1 [2]
	(b) (i) zero A1 [1]
	(ii) 0.3(0)A A1 [1]
	(c) (i) correct plots to within ± 1 mm B1 [1]
	(ii) <u>reasonable line/curve</u> through points giving current as 0.12 A allow ± 0.005 A) B1 [1]
	(iii) $V = IR$ C1 $V = 0.12 \times 5.0$ = 0.6(0)V A1 [2]
	(d) circuit acts as a potential divider/current divides/current in AC not the same as current in BC B1 resistance between A and C not equal to resistance between C and B B1 or current in wire AC $\times R$ is not equal to current in wire BC $\times R$ B1 [2] any 2 statements

Page 4	Mark Scheme: Teachers' version	Syllabus	Paper
	GCE AS/A LEVEL – May/June 2010	9702	22

7 (a) (i) either helium nucleus