

4	(a)	(i)	$R = V^2 / P$ or $P = IV$ and $V = IR$ $= (220)^2 / 2500$ $= 19.4 \Omega$ (allow 2 s.f.)	C1	A1	[2]
		(ii)	$R = \rho l / A$ $l = [19.4 \times 2.0 \times 10^{-7}] / 1.1 \times 10^{-6}$ $= 3.53 \text{ m}$ (allow 2 s.f.)	C1	C1	[3]
	(b)	(i)	$P = 625, 620$ or 630 W	A1	[1]	
		(ii)	R needs to be reduced <i>Either</i> length $\frac{1}{4}$ of original length <i>or</i> area $4\times$ greater <i>or</i> diameter $2\times$ greater	C1	A1	[2]
5	(a)	(i)	sum of e.m.f.'s = sum of p.d.'s around a loop/circuit	B1		[1]