

Section B

- 9 (a)** e.g. infinite input impedance/resistance
zero output impedance/resistance
infinite (open loop) gain
infinite bandwidth
infinite slew rate
(*any four, one mark each*)
- B4 [4]
- (b)** graph: square wave
180° phase change
amplitude 5.0 V
- M1
A1
A1 [3]
- (c)** correct symbol for LED
diodes connected correctly between V_{OUT} and earth
diodes identified correctly
(*special case: if diode symbol, not LED symbol, allow 2nd and 3rd marks to be scored*)
- M1
A1
A1 [3]

10 (a) e.g. beam is divergent/shows inverse square law