

- 8 (a) (i) either $P = V^2 / R$ or $I = 1200 / 230$ or 5.22 C1
 $R = (230 \times 230) / 1200$
 $R = 230^2 / 1200$ or $R = 230 / 5.22$ M1
 $= 44.1 \Omega$ $= 44.1 \Omega$ A0 [2]
- (ii) $R = \rho L / A$ C1
 $= (1.7 \times 10^{-8} \times 9.2 \times 2) / (\pi \times \{0.45 \times 10^{-3}\}^2)$ M1
 $= 0.492 \Omega$ A0 [2]
- (b) current = $230 / 44.6$ C1
power = $(230 / 44.6)^2 \times 44.1$ C1
= 1170 W A1 [3]
(allow full credit for solution based on potential divider)
- (c) e.g. less power dissipated in the heater / smaller p.d. across heater /
more power loss in cable / current lower B1
cable becomes heated / melts B1 [2]
(any two sensible suggestions, 1 each, max 2)
- 9 (a) nucleus emits α -particles or β -particles and/or γ -radiation B1