

4	(a) p.d. = $\frac{\text{energy transformed from electrical to other forms}}{\text{unit charge}}$	B1	
	e.m.f. = $\frac{\text{energy transformed from other forms to electrical}}{\text{unit charge}}$	B1	[2]
(b)	(i) sum of e.m.f.s (in a closed circuit) = sum of potential differences	B1	[1]
	(ii) $4.4 - 2.1 = I \times (1.8 + 5.5 + 2.3)$ $I = 0.24 \text{ A}$	M1	
		A1	[2]
	(iii) arrow (labelled) I shown anticlockwise	A1	[1]
	(iv) 1. $V = I \times R = 0.24 \times 5.5 = 1.3(2) \text{ V}$	A1	[1]
	2. $V_A = 4.4 - (I \times 2.3) = 3.8(5) \text{ V}$	A1	[1]
	3. <i>either</i> $V_B = 2.1 + (I \times 1.8)$ <i>or</i> $V_B = 3.8 - 1.3$ $= 2.5(3) \text{ V}$	C1	
		A1	[2]

Page 4	Mark Scheme: Teachers' version	Syllabus	Paper
	GCE AS/A LEVEL – October/November 2011	9702	23

5 (a) transverse waves have vibrations that are perpendicular / normal