

(allow any sensible comment based on candidate's answer for L)

				Total	[7]
8 (a)	$V/E = R/R_{\text{tot}}$	or	$0.5 = I \times 3900$	C1	
	$1.0/1.5 = R/(R + 3900)$	or	$1.0 = 0.5R/3900$	M1	
	$R = 7800\Omega.$	or	$R = 7800\Omega$	A0	[2]
(b)	$V = 1.5 \times (7800/\{7800 + 1250\})$	or	$I = 1.5/(7800 + 1250)$	C1	
	$= 1.29 \text{ V}..$	or	$V = IR = 1.29 \text{ V}$	A1	[2]
(c)	Combined resistance of R and voltmeter is 3900Ω			C1	
	reading at 0°C is 0.75 V			A1	[2]
				Total	[6]