

Question	Answer	Marks
7(a)(i)	gain is constant	M1
	for all frequencies	A1
7(a)(ii)	no time delay between input (voltage) and output (voltage)	B1
	clear reference to <u>change</u> (s) in input and/or output (voltages)	B1
7(b)	diagram: V_{IN} connected to V^+ only	B1
	midpoint between resistors R_1 and R_2 connected to V^- only	B1
7(c)(i)	-3.6 V	A1
7(c)(ii)	$(+)5.0\text{ V}$	A1

9702/41

Cambridge International AS/A Level – Mark Scheme

October/November 2018

PUBLISHED

Question	Answer	Marks
9(c)	region where there is a force	M1