

- 5 (a) Define the capacitance of a parallel plate capacitor.

.....

.....

..... [2]

- (b) Two capacitors X and Y have capacitances C_X and C_Y respectively. The capacitors are connected in parallel to a supply that has electromotive force (e.m.f.) E , as shown in Figure 5.1.

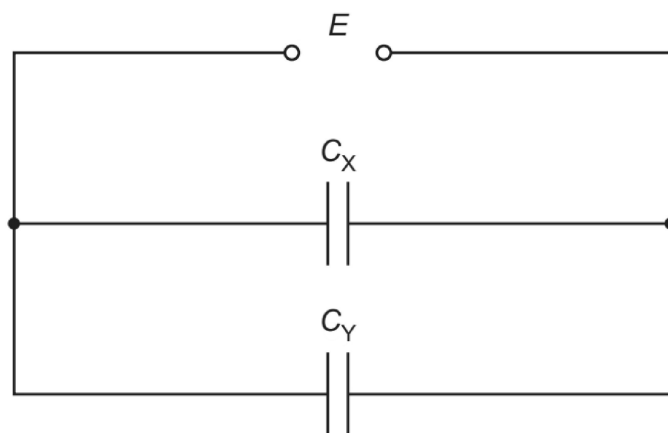


Figure 5.1

Derive the expression for the relationship between C_X , C_Y and the combined capacitance C_T of the circuit.

- (c) Two capacitors are connected in **series** to a supply that has e.m.f. 6.00 V.

One of the capacitors has capacitance C and the other has capacitance $2C$.

The total energy stored by the two capacitors is 1.30 mJ.

Calculate C in μF .

$$C = \dots\dots\dots \mu\text{F} \quad [3]$$

[Total: 8]