

11	(a)	(i)	inverting amplifier	B1	[1]
		(ii)	gain is <u>very</u> large/infinite	B1	
			V^+ is earthed/zero	B1	
			for amplifier not to saturate, P must be (almost) earth/zero	B1	[3]
	(b)	(i)	$R_A = 100\text{ k}\Omega$	A1	
			$R_B = 10\text{ k}\Omega$	A1	
			$V_{IN} = 1000\text{ mV}$	A1	[3]
		(ii)	variable range meter	B1	[1]

Page 6	Mark Scheme	Syllabus	Paper
	GCE AS/A LEVEL – May/June 2014	9702	41