

5	(a) very high/infinite resistance for negative voltages up to about 0.4 V	B1	
	resistance decreases from 0.4 V	B1	[2]
	(b) initial straight line from (0,0) into curve with decreasing gradient but not to horizontal	M1	
	repeated in negative quadrant	A1	[2]
	(c) (i) $R = 12^2 / 36 = 4.0 \Omega$	A1	
	<i>or</i>		
	$I = P / V = 36 / 12 = 3.0 \text{ A}$ and $R = 12 / 3.0 = 4.0 \Omega$	(A1)	[1]

Page 4	Mark Scheme	Syllabus	Paper
	Cambridge International AS/A Level – May/June 2015	9702	21

(ii) lost volts = $0.5 \times 2.8 = 1.4$ (V) or $E = 12 = 2.8 \times (R + r)$ C1

$R = V/I = (12 - 1.4)/2.8$ or $(R + r) = 4.29 \Omega$ C1

$= 3.8$ (3.79) Ω or $R = 3.8 \Omega$ A1 [3]

(d) resistance of the lamp increases with increase of V or I B1 [1]