

5	(a) (i)	in series $2X$ <u>or</u> in parallel $X/2$ other relationship given <u>and</u> $4\times$ greater in series (than in parallel)	M1	A1	[2]
	(ii)	due to the internal resistance	B1		
		total resistance for series circuit is not four times greater than resistance for parallel circuit	B1		[2]
	(iii)	1. $E = I_1(2X + r)$ or $12 = 1.2(2X + r)$	A1		
		2. $E = I_2(X/2 + r)$ or $12 = 3.0(X/2 + r)$	A1		[2]
	(iv)	$2X + r = 10$ and $X/2 + r = 4$ $X = 4.0\Omega$	A1		[1]

Page 4	Mark Scheme	Syllabus	Paper
	Cambridge International AS/A Level – October/November 2014	9702	22

(b) $P = I^2R$ or V^2/R or VI

C1

$$\begin{aligned}\text{ratio} &= [(1.2)^2 \times 4] / [(1.5)^2 \times 4] \\ &= 0.64\end{aligned}$$

A1 [2]

(c) the resistance (of a lamp) changes with V or I

B1

V or I is greater in parallel circuit or circuit 2
or V or I is less in series circuit or circuit 1

B1 [2]