

6	(a) internal resistance causes lost volts	B1	
	p.d. across lamp is less than 12 V, power is less than 48 W	B1	[2]
	(b) (i) greater lost volts or p.d. across cell/lamp reduced, less current in lamp	B1	[1]
	(ii) p.d. across lamp/current <u>in lamp</u> decreases, hence resistance decreases	B1	[1]