

9	(a) (i) (+) 3.0 V	B1	[1]
	(ii) potential = $6.0 \times \{2.0 / (2.0 + 2.8)\}$ = 2.5 V	C1 A1	[2]
	(iii) potential = $6.0 \times \{2.0 / (2.0 + 1.8)\}$ = 3.2 V	A1	[1]
	(b) at 10 °C, $V_A > V_B$ V_{OUT} is -9.0 V (<i>allow "negative saturation"</i>)	M1 A1	
	at 20 °C, V_{OUT} is +9.0 V (<i>if 20 °C considered initially, mark as M1,A1,B1</i>)	B1	
	sudden switch (from -9 V to +9 V) when $V_A = V_B$	B1	[4]