

7	(a) (i) $V_0 (= 14\sqrt{2}) = 19.8 (20) \text{ V}$	A1 [1]
	(ii) $\omega (= 2\pi \times 750) = 4700 \text{ rad s}^{-1}$	A1 [1]
	(b) large amount of charge required to charge capacitor capacitor would charge and discharge rapidly/in a very short time or capacitor would charge and discharge 750/1500 times per second	M1 M1
	$I = Q/t$, so large current	A1 [3]

Page 5	Mark Scheme	Syllabus	Paper
	Cambridge International AS/A Level – October/November 2015	9702	43