

7	(a)	both measure (energy / work) / charge	B1	
		for e.m.f., transfer of chemical energy to electrical energy	B1	
		for p.d., transfer of electrical energy to thermal energy / other forms	B1	[3]
(b)	(i)	$I_1 + I_2 = I_3$	B1	[1]
	(ii)	1. $E_2 = I_2 R_2 + I_3 R_3$	B1	[1]
		2. $E_1 - E_2 = I_1 R_1 - I_2 R_2$	B1	[1]