

Question	Answer	Marks
6(a)	joule/coulomb	B1
6(b)(i)	lamps have same p.d./lamps have p.d. of 2.7 V	B1
	current = $0.15 + 0.090$ $= 0.24 \text{ A}$	A1
6(b)(ii)	$R = (4.5 - 2.7) / 0.24$ or $R_P = 18 (\Omega)$ and $R_Q = 30 (\Omega)$ $1/R_T = 1/18 + 1/30$ and so $R_T = 11.25$ $4.5 = 0.24 \times (R + 11.25)$	C1
	$R = 7.5 \Omega$	A1

Question	Answer	Marks
6(b)(iii)	$R = \rho l / A$	C1
	$R_P / R_Q = [(2.7/0.15)/(2.7/0.09)] \quad (= 0.60)$	C1
	ratio = 0.60×2^2 = 2.4	A1
6(b)(iv)	less p.d. across resistor/greater p.d. across <u>P</u>	B1
	greater current through <u>P</u> and so resistance (of P) increases	B1

Question	Answer	Marks
7(a)	arrow pointing vertically down the page	B1
7(b)	$E \equiv \frac{1}{2}mv^2$	C1