

Question	Answer	Marks
7(a)	(capacitance =) charge / potential	M1
	charge is (numerically equal to) charge on one plate	A1
	potential is potential difference between plates	A1
7(b)(i)	$4.5 \times 10^{-6} \text{ C}$	A1
7(b)(ii)	$9.0 \times 10^{-8} \text{ C}$	A1
7(b)(iii)	capacitance = $(9.0 \times 10^{-8}) / 120$	C1
	$= 7.5 \times 10^{-10} \text{ F}$	A1
7(c)	total capacitance is halved	B1
	current is halved	B1

9702/41

Cambridge International AS/A Level – Mark Scheme

May/June 2018

PUBLISHED

Question	Answer	Marks
2(a)(i)	(fraction of) output is combined with the input	M1