

Question	Answer	Marks
8(a)(i)	(fraction of) output is combined with the input	M1
	output (fraction) subtracted/deducted from input	A1
8(a)(ii)	any two valid points e.g.: - greater bandwidth/gain constant over a larger range of frequencies/greater bandwidth - smaller gain	B2
8(b)(i)	gain = $(-9600/800)$	C1
	= -12	A1
8(b)(ii)	1. 1.2V	B1
	2. $-6V$	B1
8(b)(iii)	replace the 9600Ω resistor with an LDR	B1

9702/41

Cambridge International AS/A Level – Mark Scheme

May/June 2018

PUBLISHED

Question	Answer	Marks
9(c)	Using Fleming's left hand rule, force on wire is upwards	D1