

Question	Answer	Marks
7(a)(i)	(fraction of) output is combined with the input	M1
	output (fraction) <u>subtracted/deducted</u> from input	A1
7(a)(ii)	Any two valid points e.g. • greater bandwidth/gain constant over a larger range of frequencies • smaller gain	B2
7(b)(i)	gain = $1 + (6400 / 800)$ = 9.0	A1
7(b)(ii)	1. (+)5.4 V	A1
	2. –9.0 V	A1
7(b)(iii)	replace the 6400Ω resistor with a thermistor	B1

9702/42

Cambridge International AS/A Level – Mark Scheme

May/June 2018

PUBLISHED

Question	Answer	Marks
9(c)	electric and magnetic fields at right angles to one another (may be shown on a clearly labelled diagram)	D1