

Question	Answer	Marks
7(a)(i)	$(V =) 1.50 - 1.36$ $(= 0.14 \text{ V})$	B1
	$\text{current} = V / R$ $= 0.14 / 0.28 = 0.50 \text{ A}$	A1
7(a)(ii)	$\text{resistance} = V / I$	C1
	$= 1.36 / 0.50$ $= 2.7 \Omega$	A1
7(a)(iii)	$R = 2.7 - 1.0$ $= 1.7 \Omega$	A1
7(b)(i)	two resistors correctly shown in parallel with cell and no other components	B1
7(b)(ii)	(external) resistance is now smaller and (so) current (in cell) is greater / (external) resistance smaller fraction of total resistance / internal resistance larger fraction of total resistance	B1
	(greater p.d. across internal resistance so) terminal p.d. is less	B1