

- 8 (a) (i) two resistors in series B1
 (ii) two resistors in parallel B1
 (iii) any correct combination B2 [4]
 (1/2 only in (iii) if connections to external circuit not clear)
- (b) (i) $P = I^2 R$
 $0.81 = 100 I^2$ C1
 $I = 0.090 \text{ A}$ A1
 (ii) current in 25Ω resistor = 0.045 A C1
 power = 0.051 W A1 [4]